
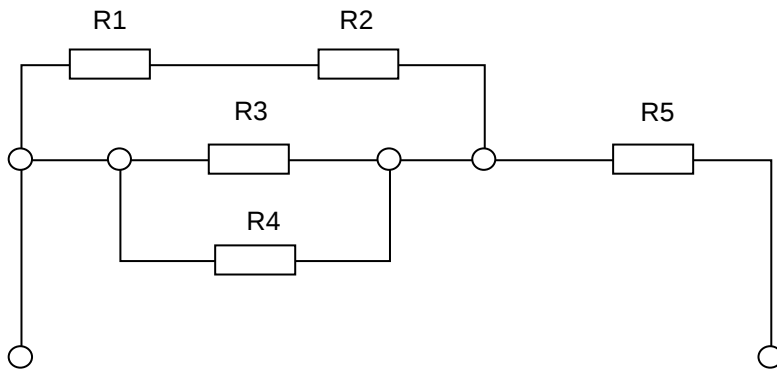


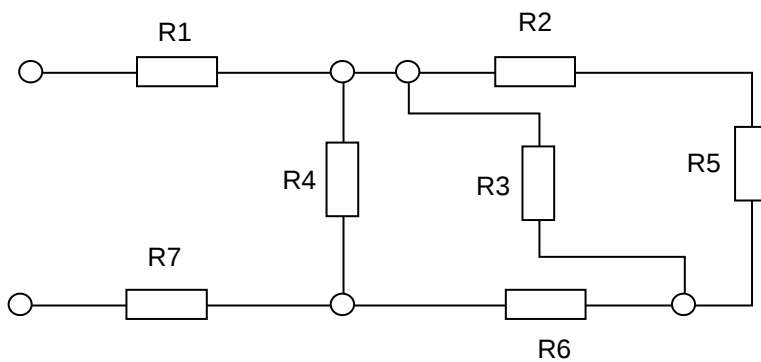
Zadání 8. 12., odevzdání 15. 12. 2024
Vypočítejte napětí a proudy na všech rezistorech



$R_1=6, R_2=8, R_3=20, R_4=15, R_5=10 \, \Omega$
 $U=20V$



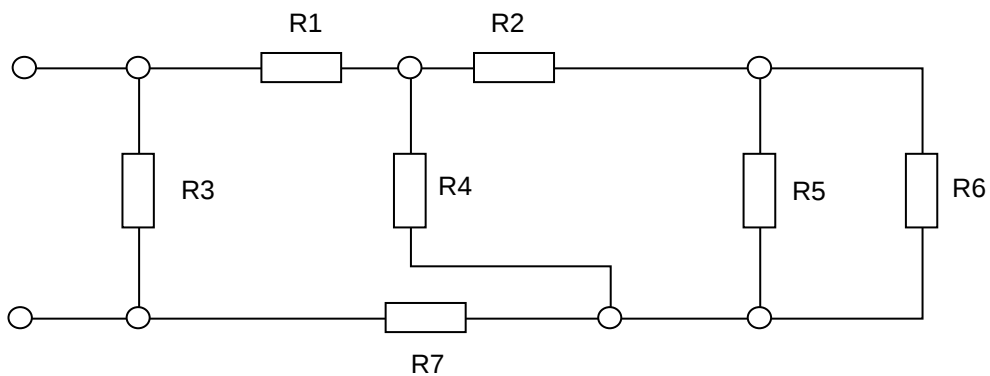$R_1=R_2=R_3=R_4=R_5=R_6=R_7=4 \, \Omega$
 $U=10V$



$R_1=R_2=R_3=R_4=R_5=R_6=R_7=8 \, \Omega$
 $U=20V$